



DECODER & ENCODER



Outline

- Decoder
 - Three-to-Eight-Line Decoder
 - Two-to-Four-line Decoder with Enable Input
- Combination of decoders
- Adder with decoders
- Encoder
 - Octal-to-Binary Encoder
 - Priority Encoder

DECODER

Decoder


A decoder is a combinational circuit that converts binary information from n input lines to a maximum of 2^n unique output lines.

If the n -bit coded information has unused combinations, the decoder may have fewer than 2^n outputs.

Decoder

- Decoders are called *n-to-m-line* decoders, where $m \leq 2^n$
- Purpose is to generate the 2^n (or fewer) minterms of n input variables
- Each combination of inputs will assert a unique output
- The name decoder is also used in conjunction with other code converters, such as a BCD-to-seven-segment decoder

Three-to-Eight-Line Decoder

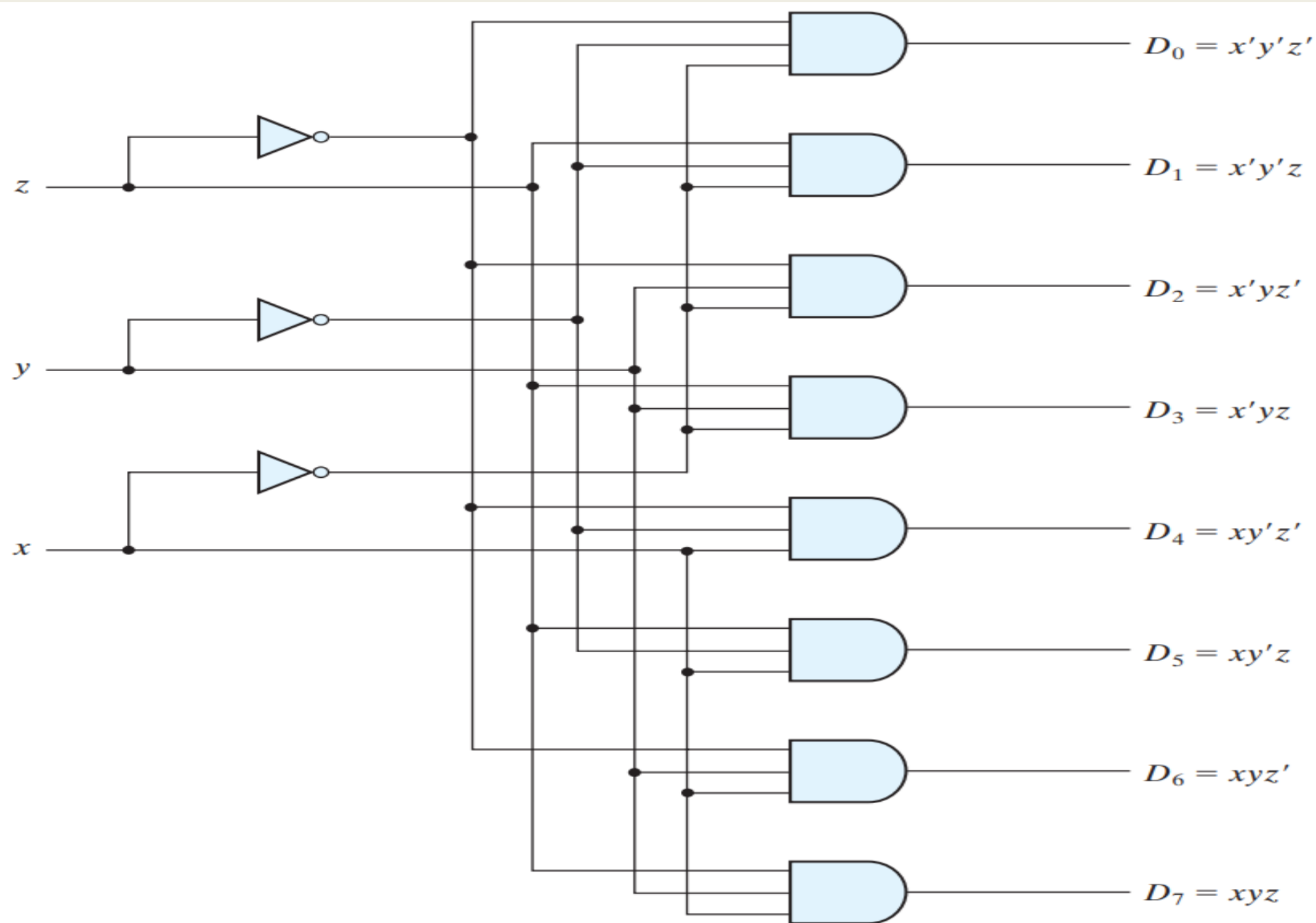

Three-to-Eight-Line Decoder

- Binary-to-octal conversion
 - The input variables represent a binary number
 - The outputs represent the eight digits of a number in the octal number system
-
- In addition, a three-to-eight-line decoder can be used for decoding any three-bit code to provide eight outputs, one for each element of the code

Three-to-Eight-Line Decoder


- For each possible input combination, there are seven outputs
 - that are equal to 0 and
 - only one that is equal to 1
- The output whose value is equal to 1 represents the minterm equivalent of the binary number currently available in the input lines.

Inputs			Outputs							
<i>x</i>	<i>y</i>	<i>z</i>	<i>D</i> ₀	<i>D</i> ₁	<i>D</i> ₂	<i>D</i> ₃	<i>D</i> ₄	<i>D</i> ₅	<i>D</i> ₆	<i>D</i> ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Two-to-four-line decoder with enable input

- Decoders include one or more enable inputs (**E**) to control the circuit operation
- Two-to-four-line decoder with an enable input constructed with NAND gates
- The decoder is enabled when E is equal to 0 (i.e., active-low enable)

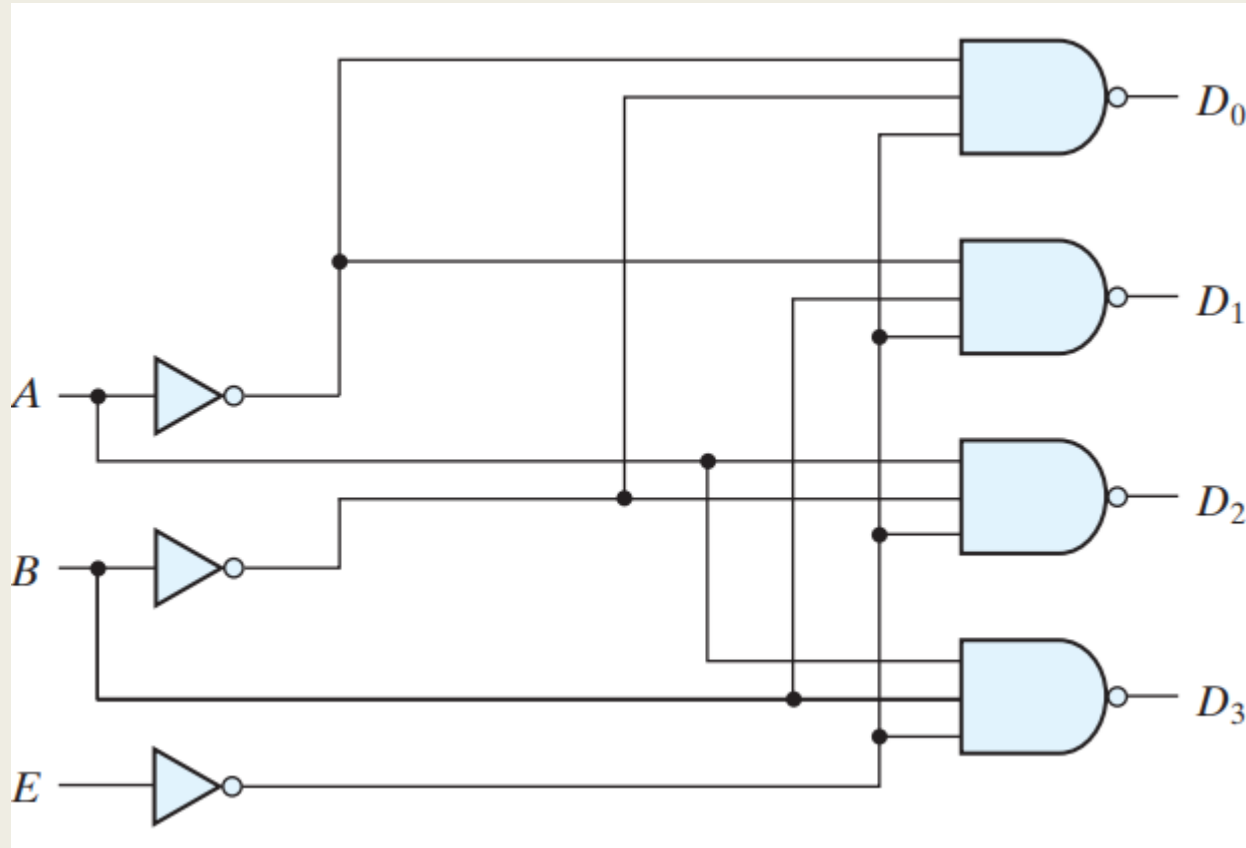Two-to-four-line decoder with enable input



E	A	B	D_0	D_1	D_2	D_3
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	1

Two-to-four-line decoder with enable input

- Only one output can be equal to 0 at any given time; all other outputs are equal to 1
- The output whose value is equal to 0 represents the minterm selected by inputs A and B
- The circuit is disabled when E is equal to 1, regardless of the values of the other two inputs

Combination of decoders

- Decoders with enable inputs can be connected together to form a larger decoder circuit.
- **Two 3-to-8-line decoders** with enable inputs connected to form a **4-to-16-line decoder**.

Case 1:


When $w=0$, the top decoder is enabled and the other is disabled.

The bottom decoder outputs are all 0's, and the top eight outputs generate minterms 0000 to 0111.

Case 2 (together with case 1):

When $w=1$, the enable conditions are reversed.

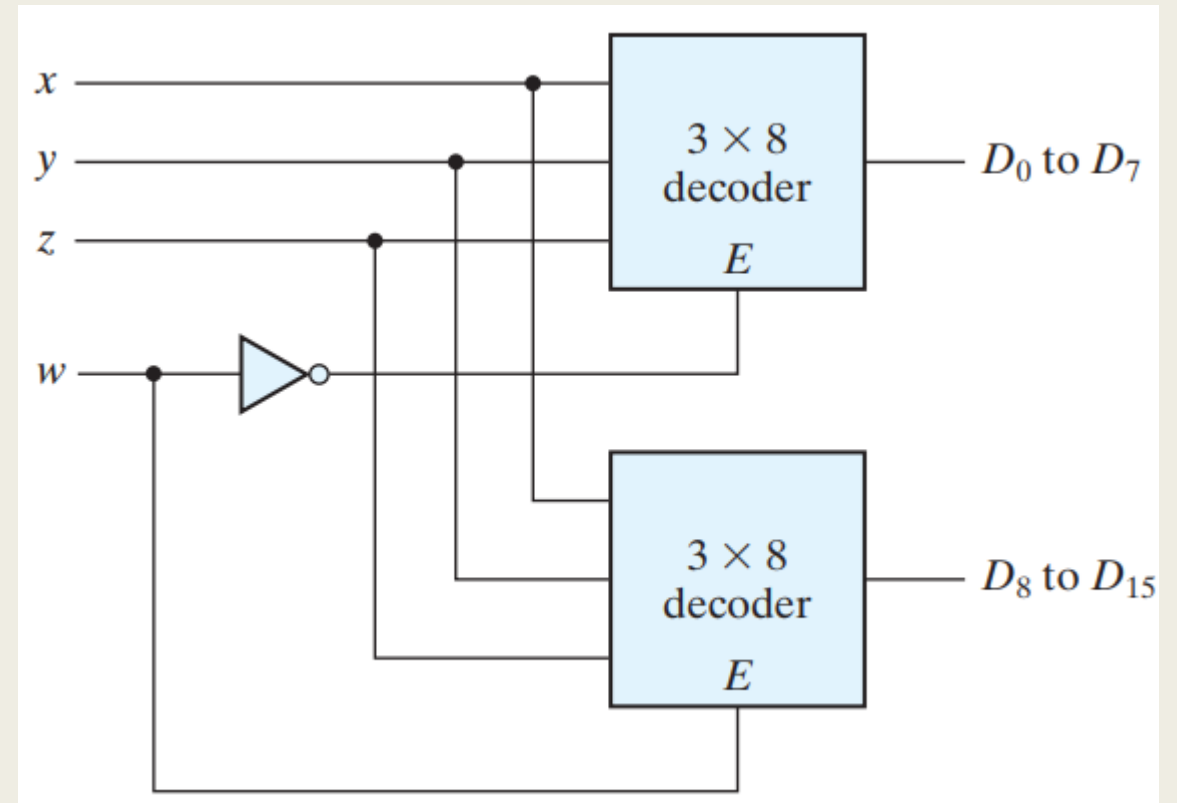The bottom decoder outputs generate minterms 1000 to 1111, while the outputs of the top decoder are all 0's.



Adder with decoder

- Decoder (with some OR gates) can be used to implement any combinational circuit, for example a Full Adder
- Truth table of Full Adder, we get

Inputs			Outputs	
X	Y	Z	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


The Canonical SOP of the output functions:

$$S(X, Y, Z) = \sum(1, 2, 4, 7)$$

$$C(X, Y, Z) = \sum(3, 5, 6, 7)$$

Adder with decoder

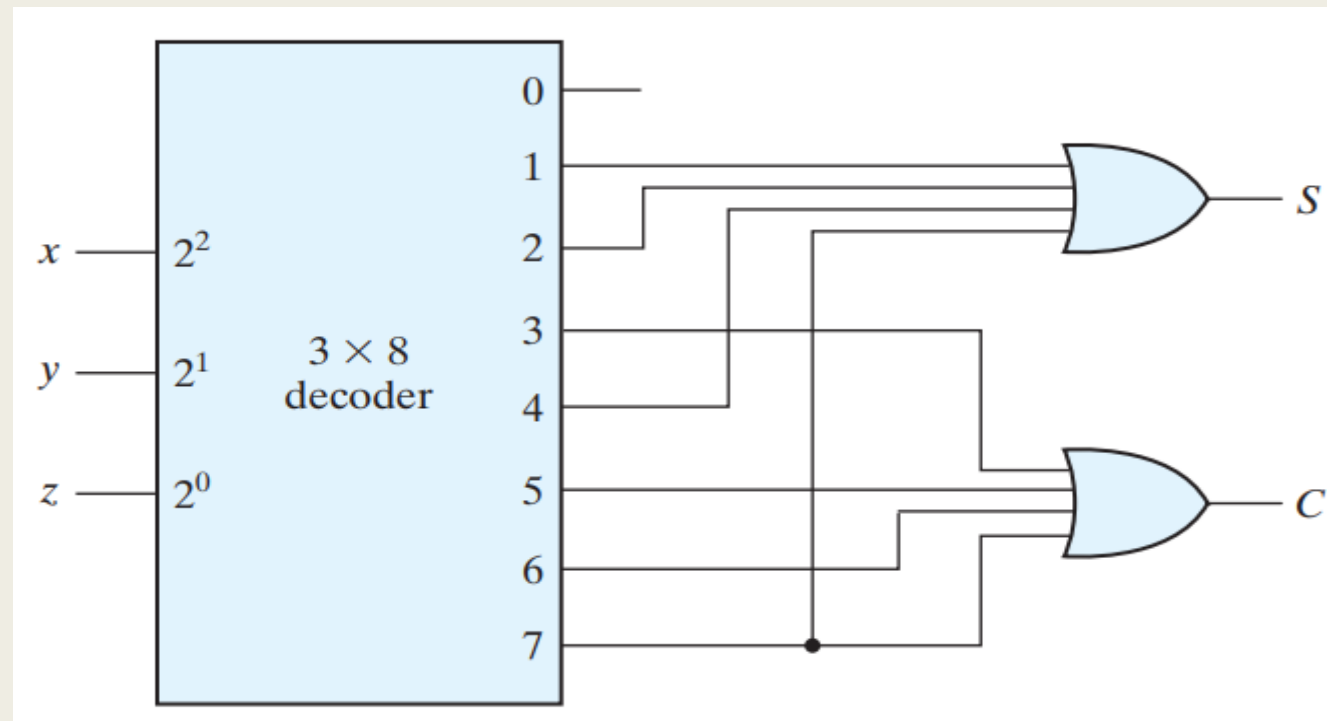- three inputs and a total of eight minterms ----- a three-to-eight-line decoder
- The decoder generates the eight minterms for x , y , and z
- The OR gate for output S forms the logical sum of minterms 1, 2, 4, and 7
- The OR gate for output C forms the logical sum of minterms 3, 5, 6, and 7



ENCODER

Encoder

- Encoder is a digital circuit that performs the inverse operation of a decoder
- An encoder has 2^n (or fewer) input lines and n output lines.
- The output lines, as an aggregate, generate the binary code corresponding to the input value
- **Example of an encoder** : the octal-to-binary encoder

Octal-to-Binary Encoder

- Eight inputs (one for each of the octal digits) and three outputs
- Outputs generate the corresponding binary number
- The encoder can be implemented with OR gates whose inputs are determined directly from the truth table
- **Main constraint:** only one input has a value of 1 at any given time.

Inputs								Outputs		
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

Boolean Output functions:

$$z = D_1 + D_3 + D_5 + D_7$$

$$y = D_2 + D_3 + D_6 + D_7$$

$$x = D_4 + D_5 + D_6 + D_7$$

Octal-to-Binary Encoder

Limitation:

- only one input can be active at any given time
- If two inputs are active simultaneously, the output produces an undefined combination.
- **Example:** if D3 and D6 are 1 simultaneously, the output of the encoder will be 111 because all three outputs are equal to 1. The output 111 does not represent either binary 3 or binary 6. **[PROBLEM !!!]**
- **SOLUTION:** encoder circuits must establish an input priority to ensure that only one input is encoded: **higher priority for inputs with higher subscript numbers**
- **Example:** if both D3 and D6 are 1 at the same time, the output will be 110 because D6 has higher priority than D3

Priority Encoder

- A priority encoder is an encoder circuit that includes the priority function.
- The operation of the priority encoder is such that if two or more inputs are equal to 1 at the same time, **the input having the highest priority will be considered**

Priority Encoder

Inputs				Outputs		
D_0	D_1	D_2	D_3	x	y	V
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

Truth table of a four-input priority encoder

- With two outputs, x and y , a third output V (**Valid bit indicator output**)
 - $V = 1$, when one or more inputs are equal to 1
 - If all inputs are 0, there is no valid input and $V=0$
- The other two outputs are not inspected when $V=0$ are specified as the **don't-care Conditions**.
- Don't Care Conditions** (Xs) in inputs are useful:
 - Instead of listing all 16 minterms of four variables, the truth table uses an X to represent either 1 or 0.
 - Example, X100 represents the two minterms 0100 and 1100.

Priority Encoder

Boolean Output functions:

$$x = D_2 + D_3$$

$$y = D_3 + D_1 D'_2$$

$$V = D_0 + D_1 + D_2 + D_3$$


$D_0 D_1$ \ $D_2 D_3$		D_2			
		00	01	11	10
D_0	00	m_0 X	m_1 1	m_3 1	m_2 1
	01	m_4	m_5 1	m_7 1	m_6 1
	11	m_{12}	m_{13} 1	m_{15} 1	m_{14} 1
	10	m_8	m_9 1	m_{11} 1	m_{10} X

$x = D_2 + D_3$

$D_0 D_1$ \ $D_2 D_3$		D_2			
		00	01	11	10
D_0	00	m_0 X	m_1 1	m_3 1	m_2
	01	m_4 1	m_5 1	m_7 1	m_6
	11	m_{12} 1	m_{13} 1	m_{15} 1	m_{14}
	10	m_8	m_9 1	m_{11} 1	m_{10}

$y = D_3 + D_1 D'_2$

Priority Encoder

 

Logic Diagram of a four-input priority encoder